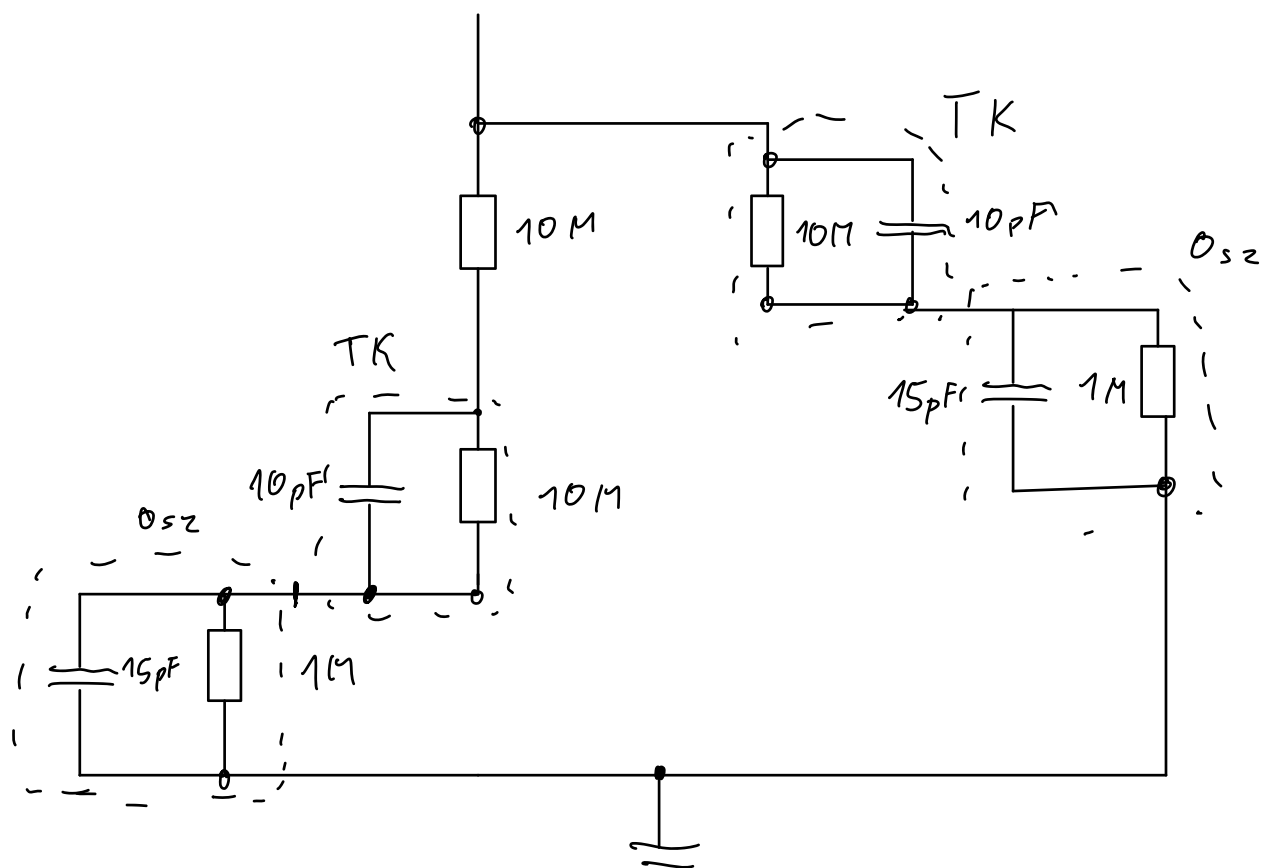




$$f = 1000 \text{ Hz} \quad T = \frac{1}{1000} \text{ s}$$

$$\frac{T}{360} \cdot 45 = T_{\varphi} =$$

$$\varphi = 45^\circ$$

$$133 \mu\text{s}$$

$$f = 1000 \text{ Hz} \quad T = \frac{1}{f}$$

$$\Delta T =$$

$$\frac{T}{360} \cdot \varphi = \Delta T$$

$$\varphi = \Delta T \cdot 360 \cdot f$$

$$\tau = \frac{1}{2\pi f_g} = \frac{1}{2000\pi}$$

$$10k\Omega$$

$$RC = \tau$$

$$C = \tau \cdot \frac{1}{R} = \frac{1}{2000\pi} \cdot \frac{1}{10000}$$

$$C = 15,9 \cdot 10^{-9} F = 15,9 nF$$

$$\frac{U}{I} = R = \frac{5}{0,200 \cdot 10^{-3}} = 25k$$

$$RC = \tau$$

$$C = \frac{\tau}{R} = \frac{1}{2000\pi} \cdot \frac{1}{25000}$$

$$C = 6,366 \cdot 10^{-9} F$$

$$f_c = \frac{1}{2\pi R_1 C_1} \Rightarrow R_1 C_1 = \tau = \frac{1}{2\pi f_c} = \frac{1}{2\pi \cdot 1050 Hz} = 151,576 \mu s$$

$$DCgain = \left(1 + \frac{R_2}{R_3}\right) \Rightarrow 7,7 = \left(1 + \frac{R_2}{R_3}\right)$$

$$10\mu s$$